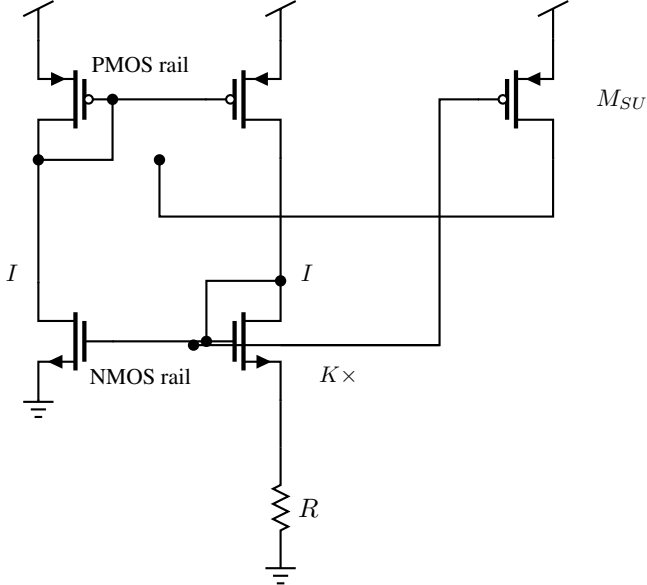




The loop only says the two branches must agree, and zero current in both agrees just as well. A startup device is not optional: without it the reference may never wake up.