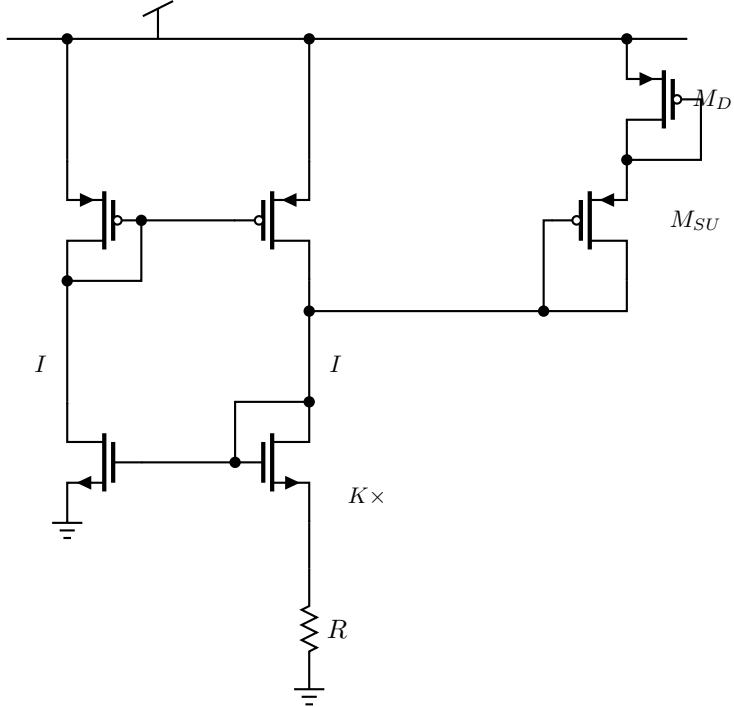




The loop only says the two branches must agree, and zero current in both agrees just as well, so a startup device is not optional. M_{SU} lifts the NMOS rail off ground until the loop takes over. M_D costs it a threshold of drive, which is what makes it let go afterwards instead of leaking into a small branch current for ever.